

ALU/Ripple Adder

- o Embedded Systems
- o Lab Report #2
- o Fareen Pourmousavian
- o 3/7/19

- Purpose

- o The purpose of this lab is to not only create a 4-bit ripple adder but to also design an ALU.


- For Each Part

- o Theory of Operation


- ♣ For the ripple adder, given inputs A and B for each bit of the 4-bit adder it should return correct sum and carry-out values. ALU should work

- ♣ I am expecting the 4-bit adder to work after doing the simulations. For the ALU, I am expecting the ALU to work on the board.

- o Schematic Diagram (as desired)

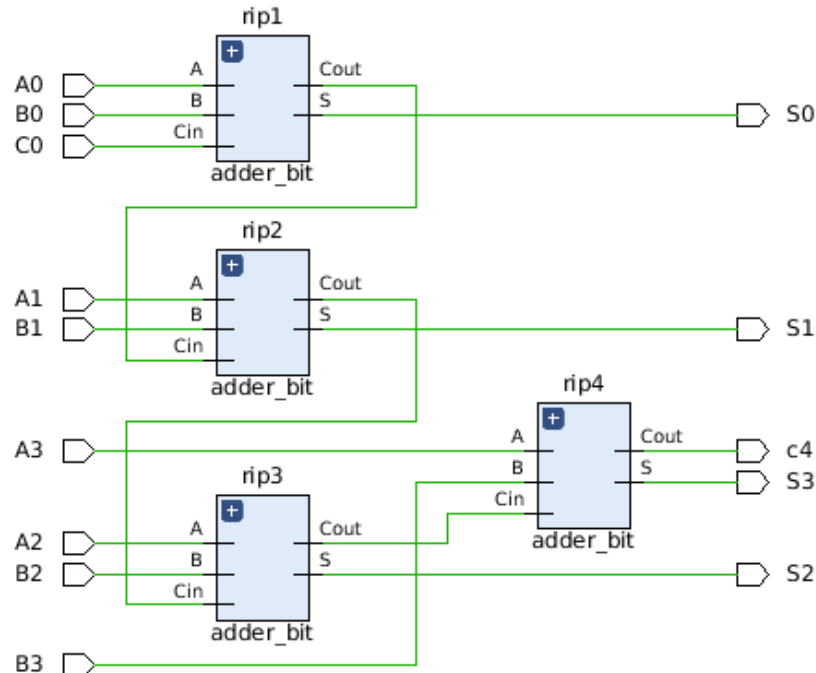

ALU_Tester

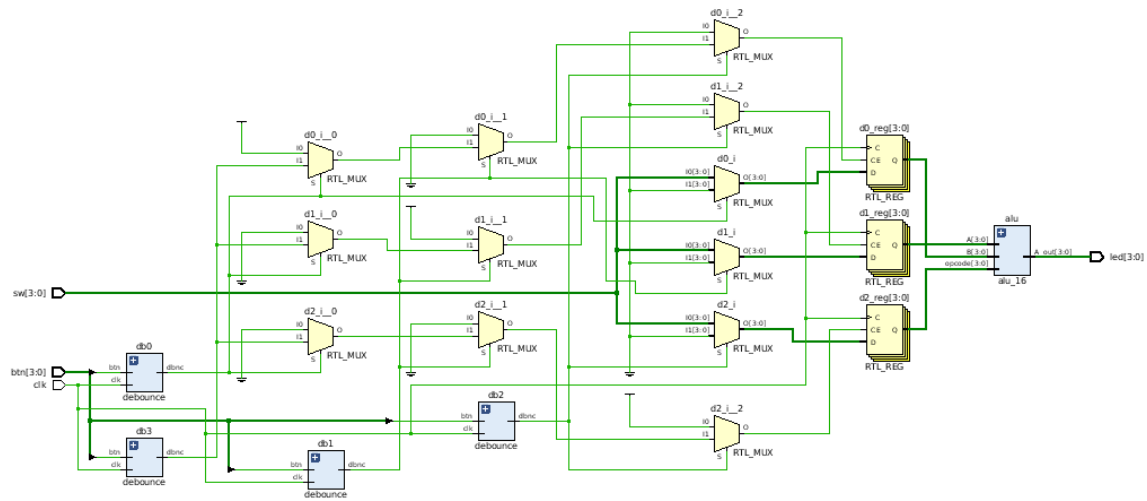

Design:

library IEEE;

use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity adder_bit is

port(A,B,Cin :in std_logic;

S,Cout :out std_logic);

end adder_bit;

architecture Adder of adder_bit is

signal F_x, top_an,bot_an :std_logic;

begin

F_x<= A XOR B;

bot_an <= A AND B;

S<=Cin XOR F_x;

COUT<= bot_an OR (Cin and F_x);

end adder;

library IEEE;

use ieee.std_logic_1164.all, ieee.numeric_std.all;

Entity ripple_4 is

port(A0,A1,A2,A3,B0,B1,B2,B3,C0:in std_logic;

c4,S0,S1,S2,S3:out std_logic);

end ripple_4;

architecture crt4 of ripple_4 is

component adder_bit

```
port(A,B,Cin :in std_logic;  
      S,Cout :out std_logic);  
end component;
```

```
signal C1,C2,C3: std_logic;  
begin
```

```
rip1 : adder_bit
```

```
port map(A=>A0,  
          B=>B0,  
          Cin=>c0,  
          S=>S0,  
          Cout=>C1);
```

```
rip2 : adder_bit
```

```
port map(A=>A1,  
          B=>B1,  
          Cin=>c1,  
          S=>S1,  
          Cout=>C2);
```

```
rip3 : adder_bit
```

```
port map(A=>A2,  
          B=>B2,  
          Cin=>c2,  
          S=>S2,  
          Cout=>C3);
```

```
rip4 : adder_bit
```

```
port map(A=>A3,  
          B=>B3,
```

```

        Cin=>c3,
        S=>S3,
        Cout=>C4);

end crt4;

library ieee;
use ieee.std_logic_1164.all,ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;

entity alu_16 is
port(A,B,opcode :in std_logic_vector(3 downto 0);
     A_out: out std_logic_vector(3 downto 0));
end alu_16;

architecture alu_func of alu_16 is
signal g_t : std_logic_vector(3 downto 0);
begin

    process(opcode)
    begin
        if (A>B) then
            g_t<="0001";
        else
            g_t<="0000";
        end if;
        case(opcode,A,B) is
            when "0000" => A_out <=A+B;

```

```

when "0001"=> A_out <= A-B;
when "0010"=>A_out<=A+1;
when "0011" => A_out<=A-1;
when "0100" => A_out<=0-A;
when "0101"=> A_out <= g_t;
when "0110"=> A_out <= A(2 downto 0)&"0";
when "0111"=> A_out <= "0"&A(3 downto 1);
when "1000"=> A_out <= "1"&A(3 downto 1);
when "1001"=> A_out <= Not(A);
when "1010"=> A_out <= A AND B;
when "1011"=>A_out <= A OR B;
when "1100" => A_out <=A XOR B;
when "1101" => A_out <=A XNOR B;
when "1110"=> A_out <=A NAND B;
when "1111" => A_out <=A NOR B;
when others => A_Out <= "0000";

end case;

end process;

end alu_func;

```

```

library ieee;

use ieee.std_logic_1164.all, ieee.numeric_std.all, ieee.std_logic_unsigned.all;

```

```

entity alu_top is
port(clk : in std_logic;
      btn,sw : in std_logic_vector(3 downto 0);
      led : out std_logic_vector(3 downto 0));

```

```

end alu_top;

architecture alu_tester of alu_top is
component alu_16
port(A,B,opcode :in std_logic_vector(3 downto 0);
      A_out: out std_logic_vector(3 downto 0));
end component;tianyi.zhang29@rutgers.edu
component debounce
port (clk : in std_logic;
      btn : in std_logic;
      dbnc : out std_logic);
end component;

signal db3_rt,db2_op, db1_A, db0_b :std_logic;
signal d3,d2,d1,d0 : std_logic_vector(3 downto 0);
begin

process(clk)
begin
    if(rising_edge(clk)) then
        if(db2_op='1') then
            d2<=sw;
        elsif(db1_A='1') then
            d1<=sw;
        elsif(db0_B='1') then
            d0<=sw;
        elsif(db3_rt='1') then
            d3<="0000";
        end if;
    end if;
end process;
end alu_tester;

```

```

        d2<="0000";

        d1<="0000";

        d0<="0000";

    end if;

end if;

end process;

```

o Test

♣ Test bench VHDL

Library IEEE;

use IEEE.std_logic_1164.all,IEEE.numeric_std.all;

ENTITY rip_t IS

END rip_t;

architecture rip of rip_t is

Component ripple_4

port(A0,A1,A2,A3,B0,B1,B2,B3,C0:in std_logic;

c4,S0,S1,S2,S3:out std_logic);

end Component;

signal A0_t,A1_t,A2_t,A3_t,B0_t,B1_t,B2_t,B3_t,C0_t : std_logic ;

signal c4_t,S0_t,S1_t,S2_t,S3_t: std_logic;

constant clk_period : time := 10 ns;

begin


```
uut: ripple_4 PORT MAP (
```

```
  A0 => A0_t,
```

```
  b0=>b0_t,
```

```
  C0=>c0_t,
```

```
  s0=>s0_t,
```

```
  A1 => A1_t,
```

```
  b1=>b1_t,
```

```
  s1=>s1_t,
```

```
  b2=>b2_t,
```

```
  A2 => a2_t,
```

```
  s2=>s2_t,
```

```
  a3=>a3_t,
```

```
  b3=>b3_t,
```

```
  c4=>C4_t,
```

```
  s3=>s3_t);
```

```
--clk_process :process
```

```
--begin
```

```
--clk_test <= '0';
```

```
--wait for clk_period/2;
```

```
--clk_test <= '1';
```

```
--wait for clk_period/2;
```

```
--end process;
```

```
stim_proc: process
```

```
begin
```


```

wait for 100ns;
A0_t<='1';
B0_t<='1';
c0_t<='0';
A1_t<='1';
B1_t<='1';
A2_t<='1';
B2_t<='1';
A3_t<='1';
B3_t<='1';
wait for 10ns;
wait;
end process;
end;



```

♣ simulation results (screen shots)


4-bit ripple adder

 

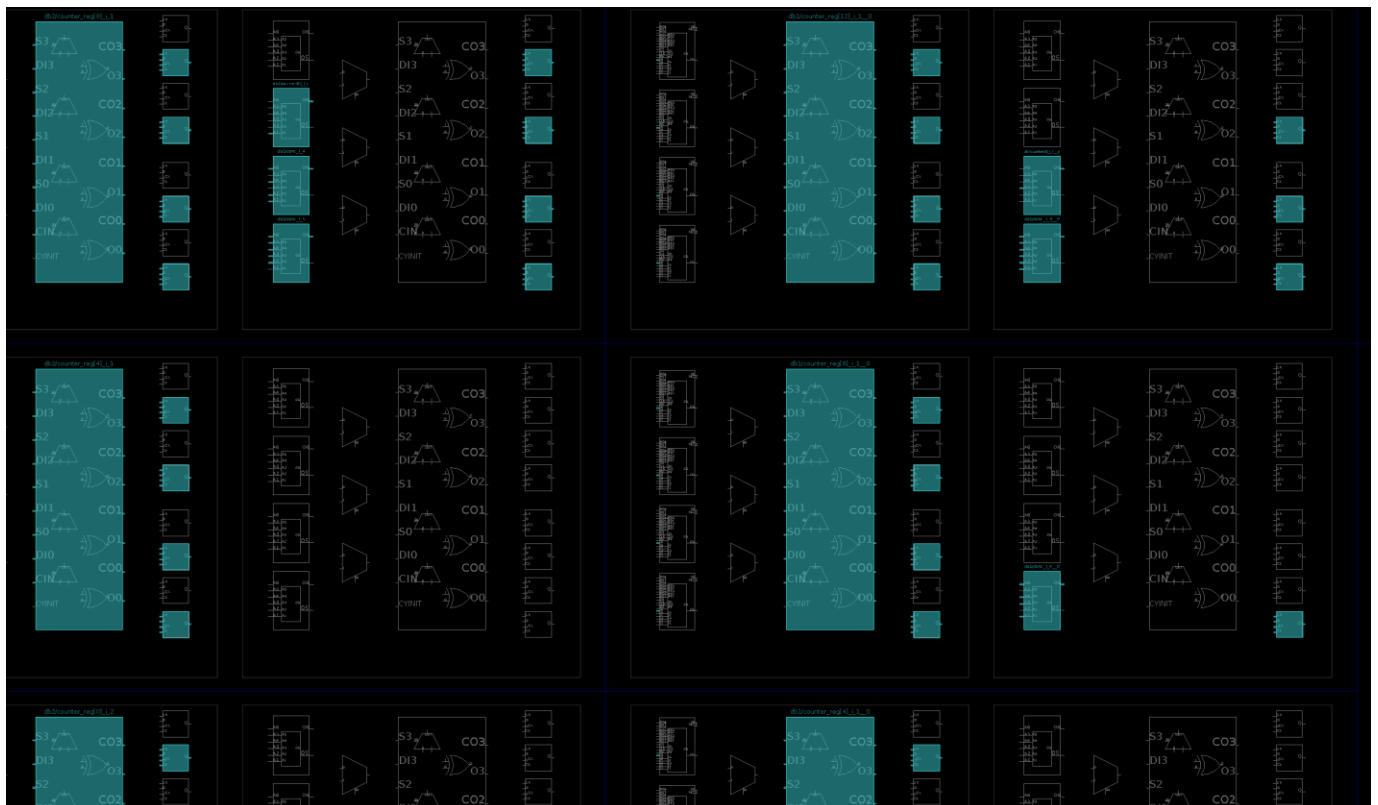 
o Implementation (If required to demo on board)



♣ Vivado Elaboration Schematic

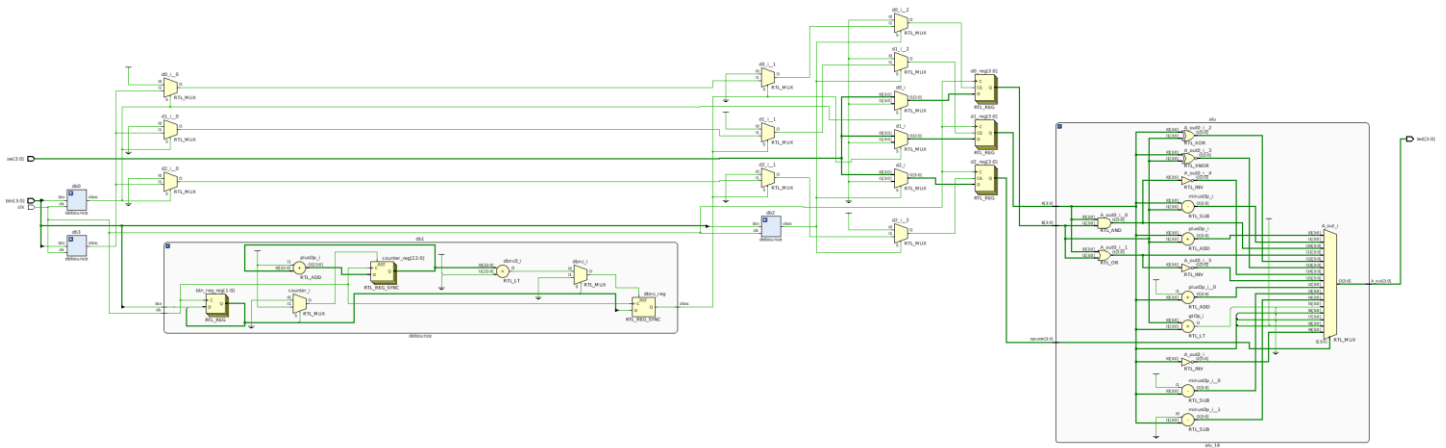


♣ Vivado Synthesis Schematic

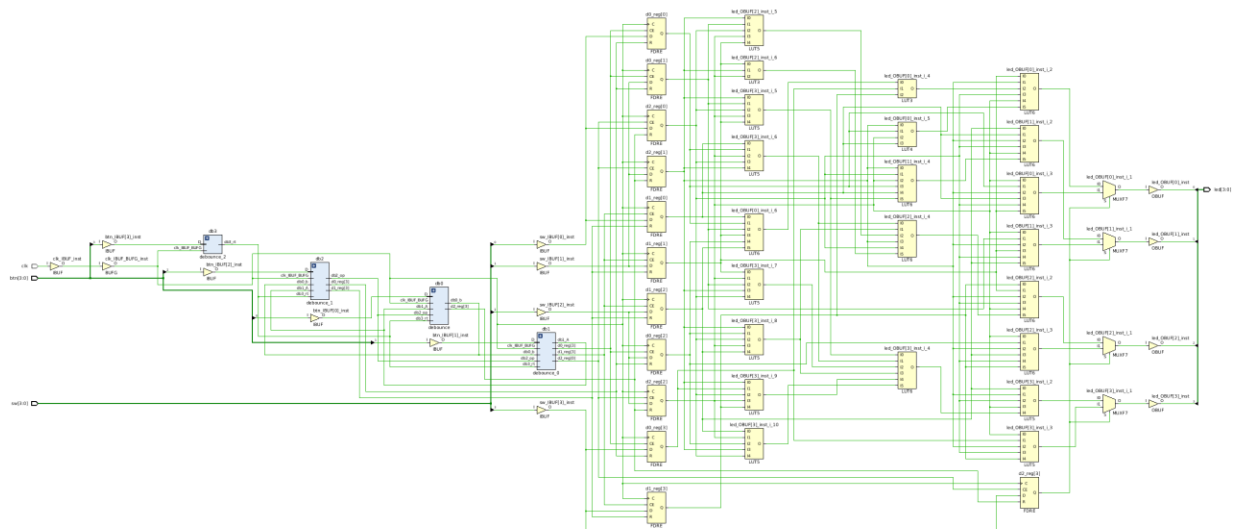

♣ Vivado Project Summary Images

• Post-Synthesis Utilization Table

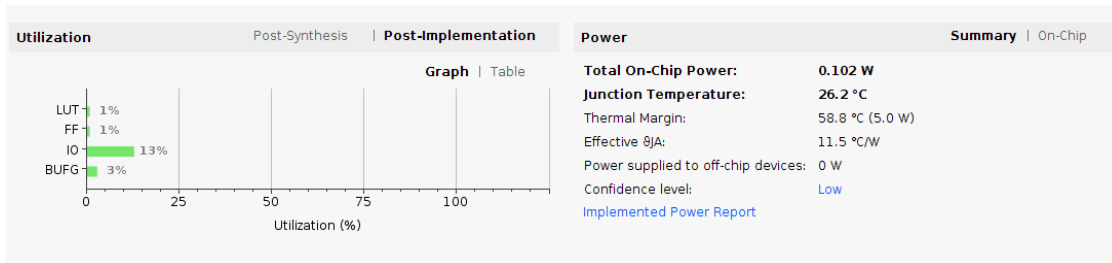

• On-chip Power Graphs


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.102 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.2°C
 Thermal Margin: 58.8°C (5.0 W)
 Effective θ_{JA} : 11.5°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

ZYBO_Master.xdc

• The only things that needed to be changed was the uncommenting of all the LED, Switches, buttons and clock signals so that those ports on the board would work when I try to implement my alu design on the board.

• Discussion


PreLab


A	B	Cin	Y	Cout
0	0	0	0	0

0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\oplus \oplus Y = A \oplus B \oplus C$$
 
$$C_{out} = AB + AC_{in} + BC_{in} = AB + C_{in}(A+B)$$



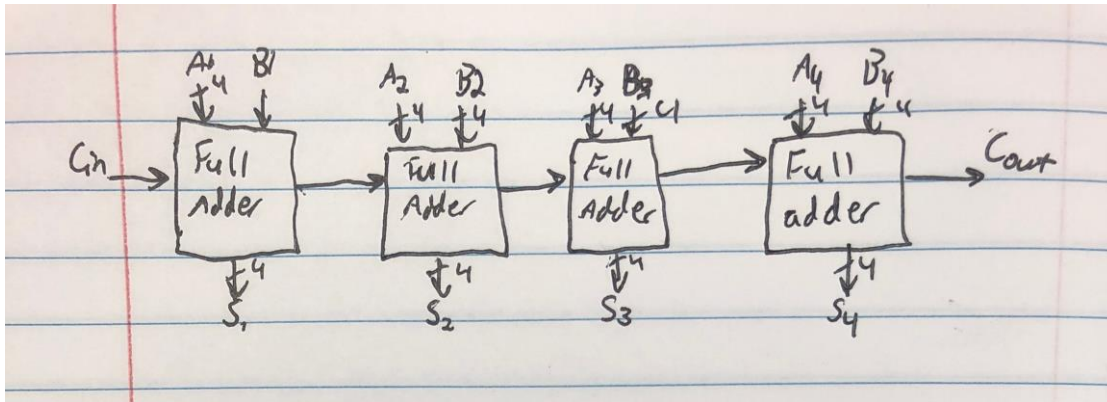

What did you learn?

- ♣ I learned what the functions of the ALU are and what they do based on a given opcode.

o Questions / Follow Up

- ♣ This lab manual made everything easy to understand and implement. I understand the ALU executes a function depending on a given op code. I completely understand ripple and full adders and how they add two numbers together by looking at their bits.

- ♣ I had a little confusion on how to connect switches to buttons to inputs of ALU because debouncers have std_logic outputs while switches and alu are std_logic_vectors